

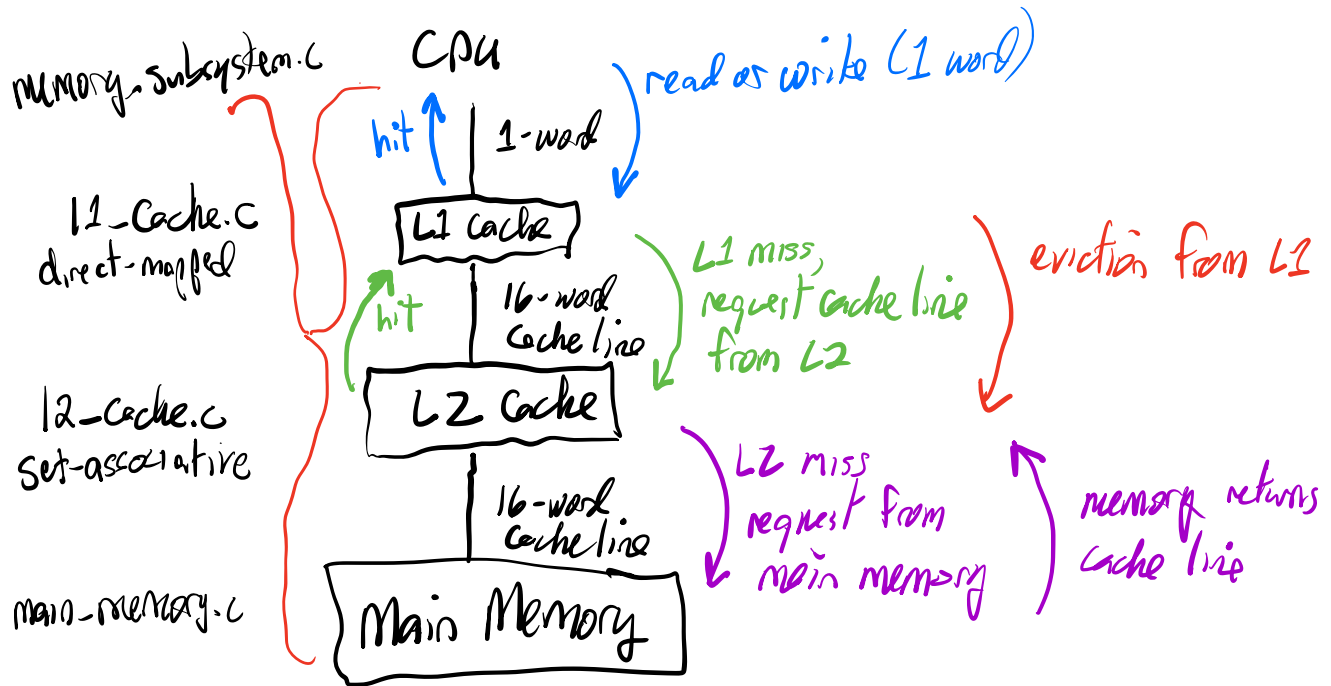



Cache Project

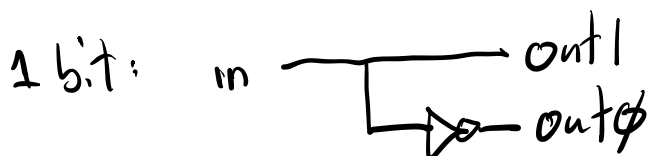

Back to digital logic:

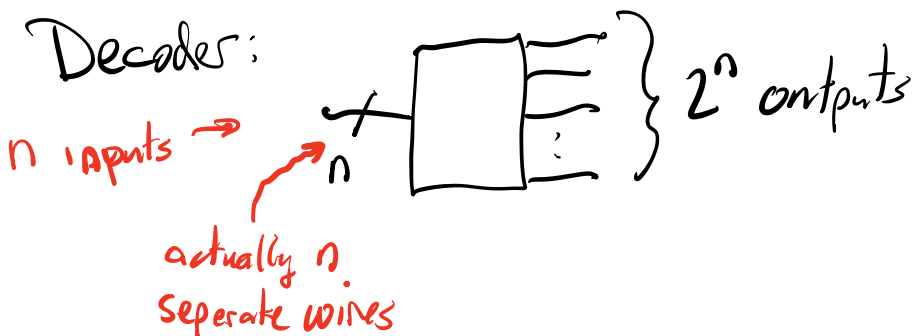

2 bit:

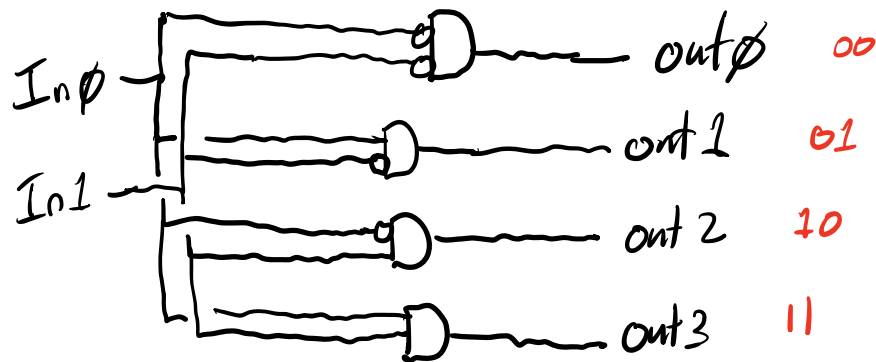

"Multiplexer" (multiplexor) "max"


- selects one of the inputs to send to the output



The n -bit selector selects one of the 2^n inputs to send to the output.


If the value of the selector is i , then the output gets the value of input i .

2-input max (1 selector input)

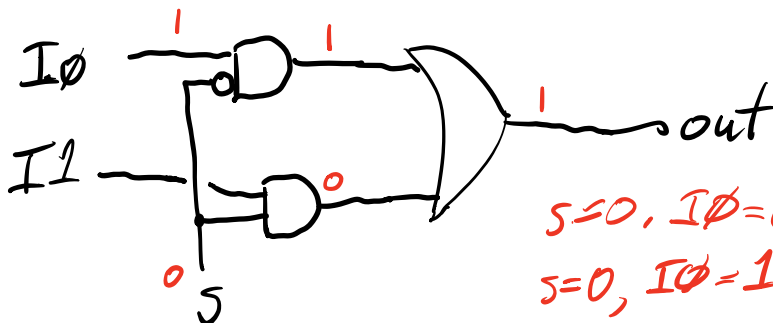


$s=0, I_0=0 \Rightarrow out=0$
 $s=0, I_0=1 \Rightarrow out=1$


4-input mux (2 selector lines)

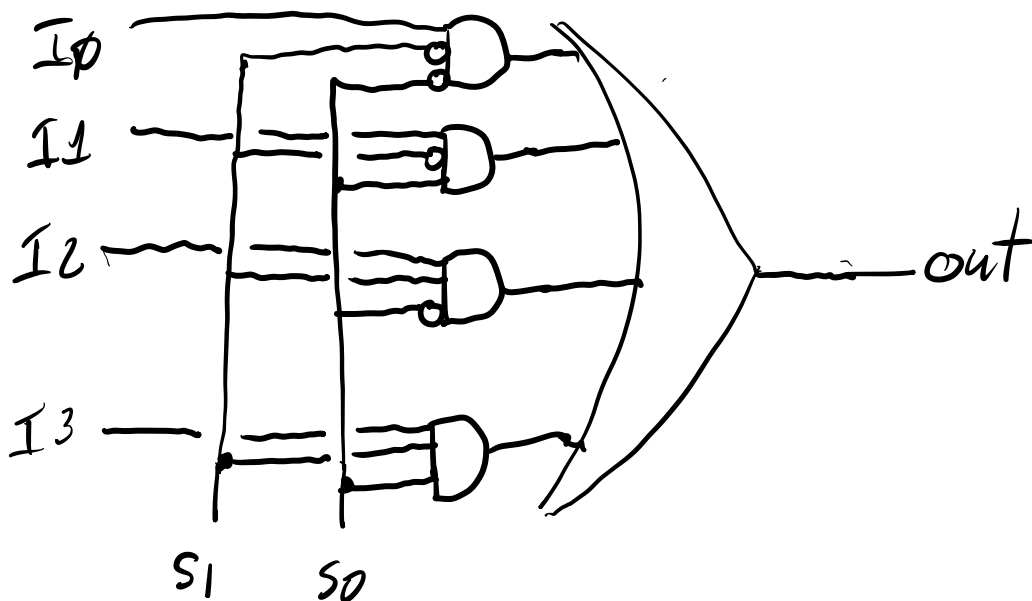

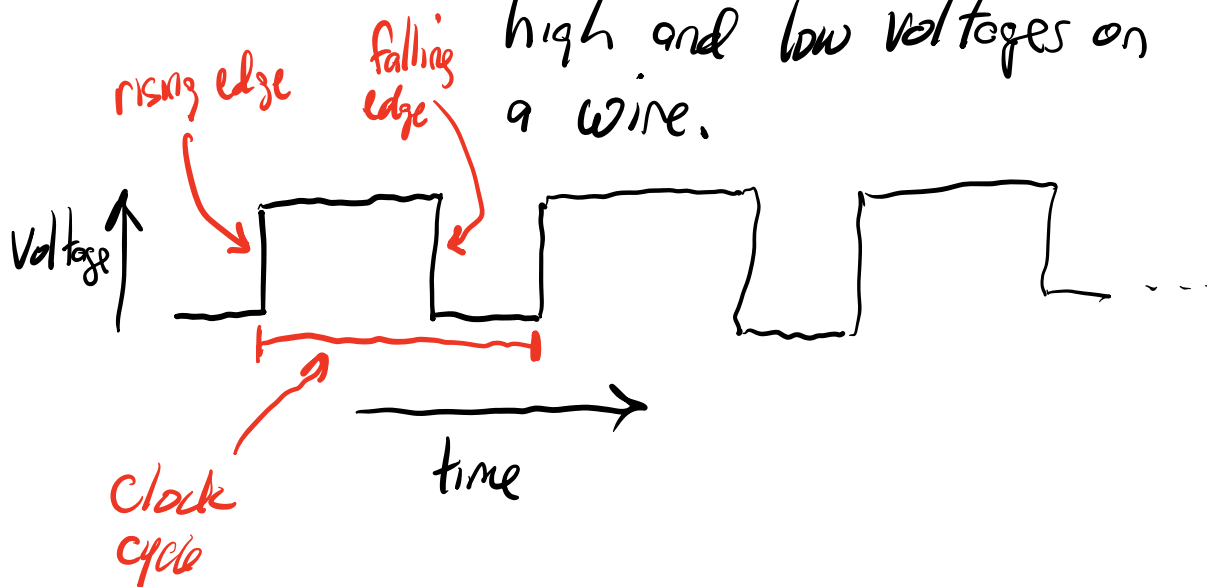
Clock - device that puts alternating high and low voltages on a wire.



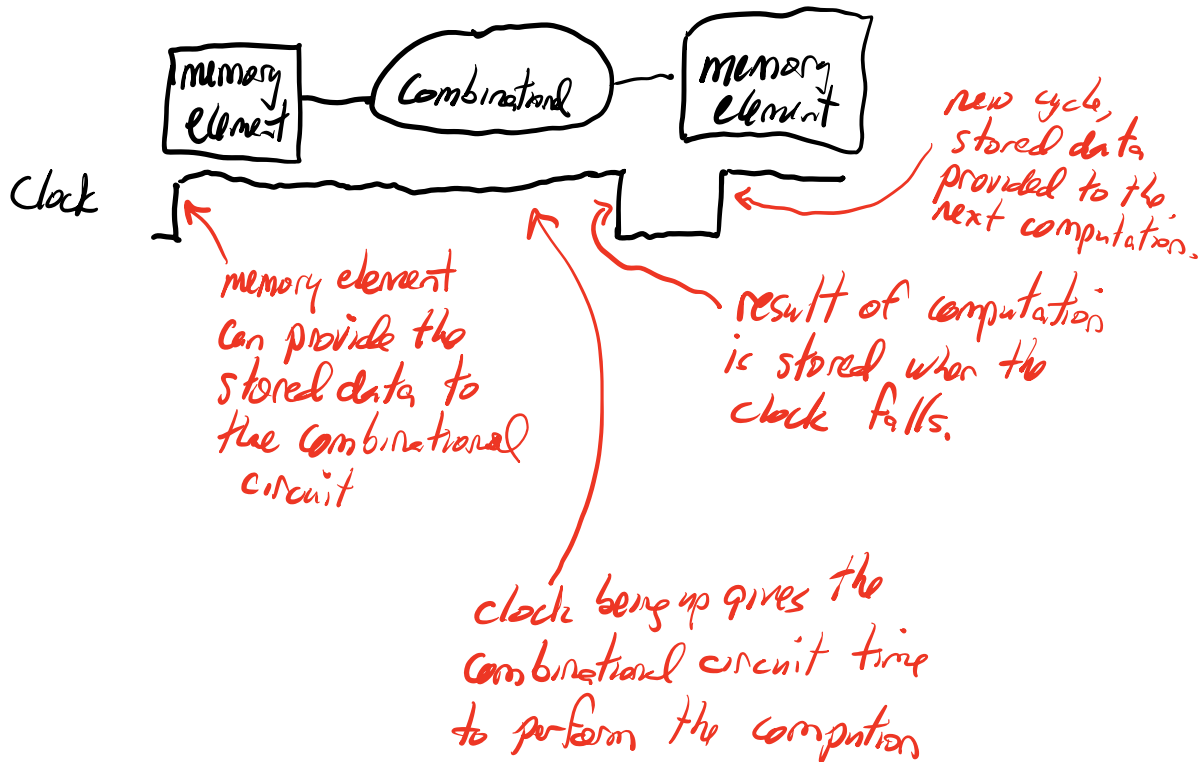A clock is needed to synchronise actions
in a circuit
- particularly the storing of data.




More realistically:

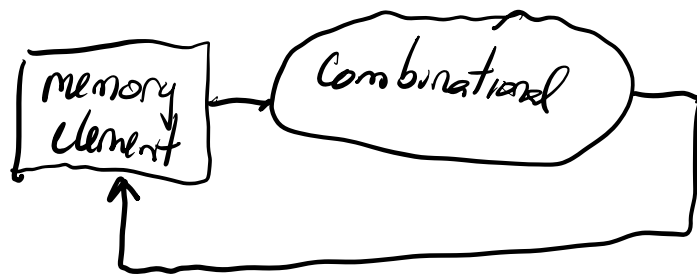

The clock prevents the overwriting
of the memory element with the
output of the combinational circuit
until the computation has finished

Memory Elements (sequential circuits)

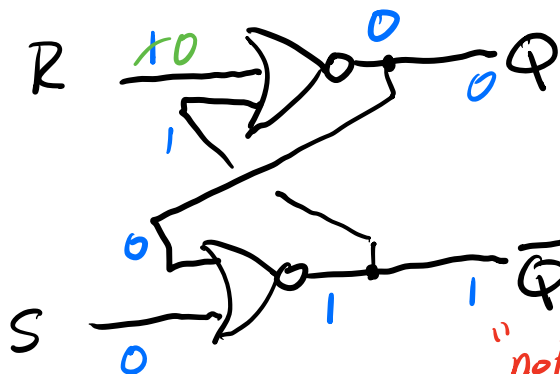"unclocked latch" (aka S-R latch for "set-reset")



$$S=1, R=0 \rightarrow Q=1, \bar{Q}=0$$

$$S=0, R=1 \rightarrow Q=0, \bar{Q}=1$$

$$S=0, R=0 \rightarrow$$

① when Q was 1 and \bar{Q} was 0
 $\rightarrow Q$ is still 1 and \bar{Q} is still 0.

② when Q was 0 and \bar{Q} was 1
 $\rightarrow Q$ is still 0 and \bar{Q} is still 1.

No change

$$S=1, R=1 \rightarrow \text{unstable state} \\ \text{- never used.}$$

When $S=0$ and $R=0$, the latch outputs will remain the same

- i.e. their value immediately before S and R both became 0.