

In a DRAM cell, reading the capacitor changes the capacitor's voltage level.

- value is wiped out
- after reading the value, the hardware has to write that value back to the capacitor.

Capacitors also "leak"

- they lose their charge over time.
- hardware has to periodically read every DRAM cell and write its value back to it.


"refresh"

- happens every 64ms
 - roughly a 0.4% overhead.
- this dynamic refresh process is why DRAM is "dynamic" RAM.

- SRAM doesn't need refreshing

"static" RAM

 Main memory is a huge array of DRAM cells:




ALU - "arithmetic logic unit"

- performs the arithmetic and logic operations.

- combinational circuit - performs computations using gates, doesn't store anything.

Constructing a simple ALU:


1-bit ALU performing AND and OR

 


Performing addition:

1-bit adder:

 - inputs: carry-in, a , b
- outs: result, carry-out




 Result = 1 when exactly one input is 1
or all three inputs are 1.




Carry Out:

 
Carry out = 1 when at least two inputs are 1.



Draw the 1-bit adder

 

1-bit ALU w/ AND, OR, +

 


64-bit ALU

- bitwise AND, OR


- 64-bit addition

- just chain together 64 1-bit ALUs.

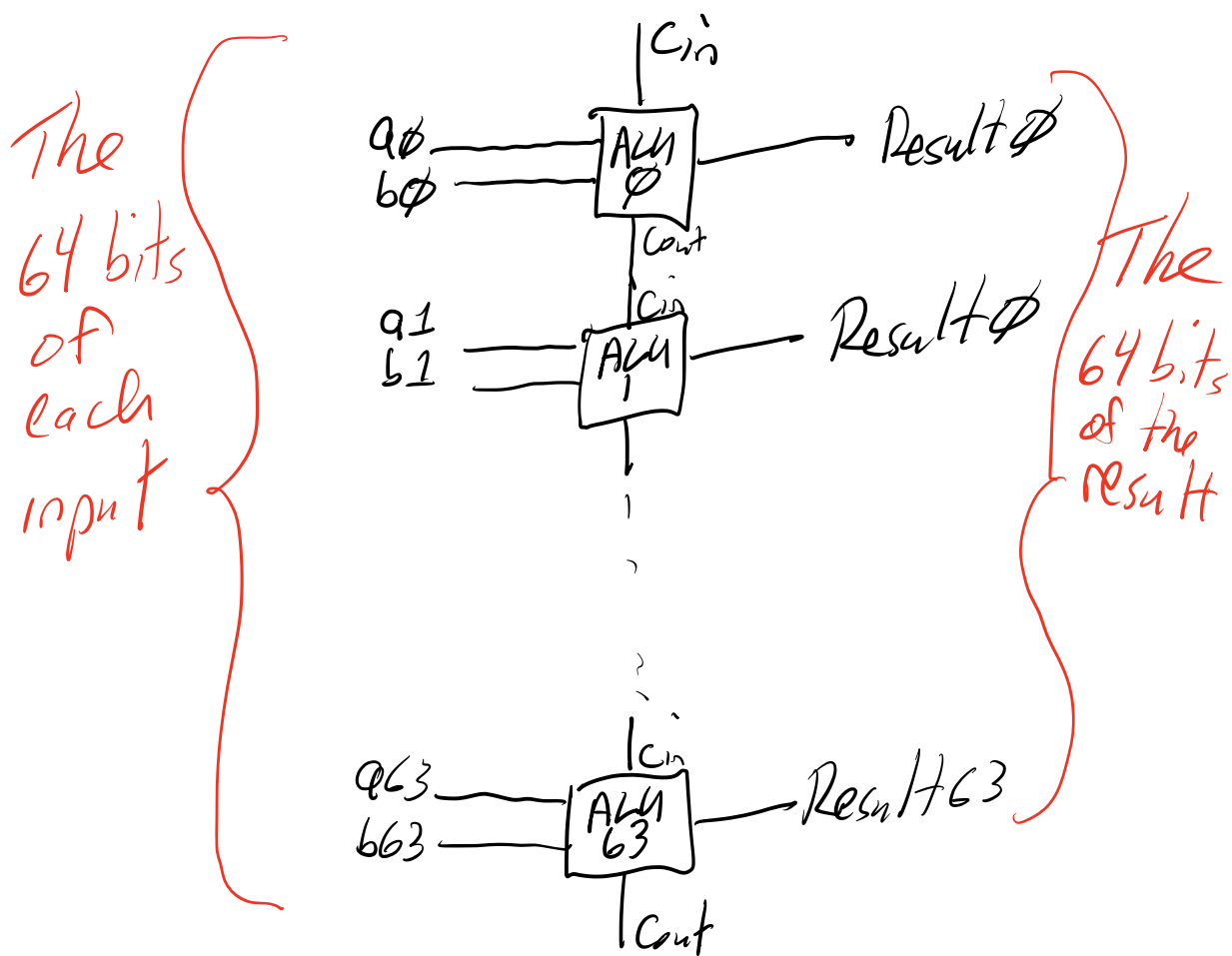

The Cont from an ALU is the Cin to the next ALU.
 - "ripple adder"

We draw an ALU as:

 

What about subtraction?

- really easy, thanks to 2 's complement!

$$a - b = a + (-b) = a + (\overline{b+1})$$


$$= (q + \bar{b}) + 1$$

use the
adder

flip bits
of b

set Carry In to 1.

 1-bit ALU with addition, subtraction,
and, or



Addition:

$$b_{\text{invert}} = 0$$

$$C_{10} = 0$$

Subtraction:

$$b_{\text{rent}} = 1$$

$$C_{in} = 1$$

The processor datapath


- how the data flows through the processor to support instructions.

The processor control specifies the values of multiplexer select lines, binvent, etc.

- not discussed here.

Portion of the datapath for fetching an instruction:

 - uses a program counter (PC)
 - special register containing the address of the next instruction.
 - aka "instruction pointer"
 - %rip



Assume every instruction is 8 bytes (64-bits)

After each instruction,

$$PC \leftarrow PC + 8$$

to point to the next instruction.

clock makes sure the PC isn't overwritten prematurely.