
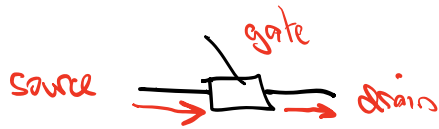



Transistors:

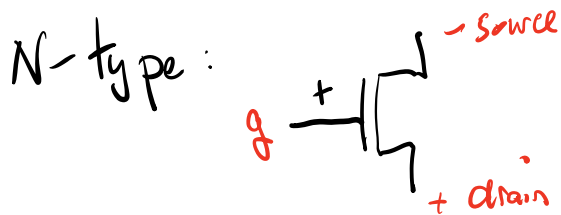

CMOS transistors - complementary metal oxide
semi conductor
sometimes it conducts, sometimes not.



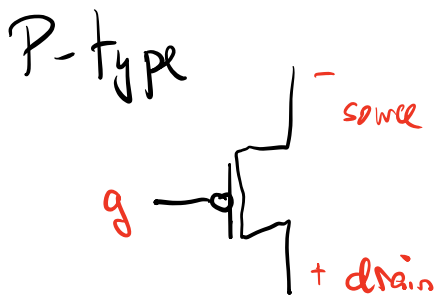
When voltage is applied at the gate, current flows from the source to the drain.



When there is low voltage at g , current will flow from the source to the drain.

- When voltage is applied at g , no current will flow from source to drain.

Building an inverter from transistors

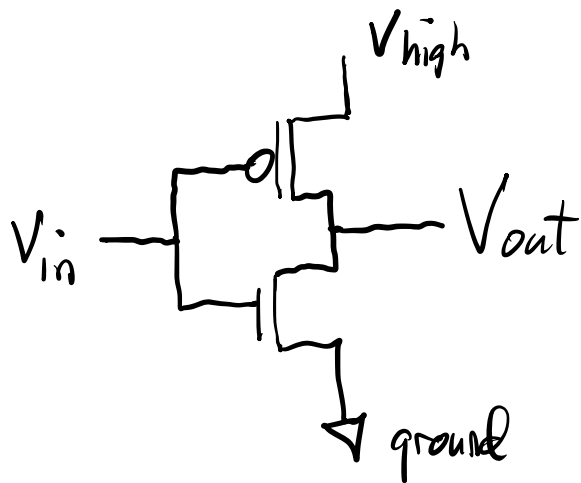

V_{in} is high: V_{out} will be low.


- high voltage represents 1, low voltage represents 0

- so $V_{in} = 1$, $V_{out} = 0$


V_{in} is low: V_{out} is high

- $V_{in} = 0$, $V_{out} = 1$

This is the boolean "NOT" operation,


 NOT GATE

Other gates:

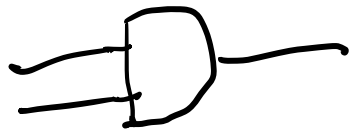

AND Gate

- output is 1 when both inputs are 1.

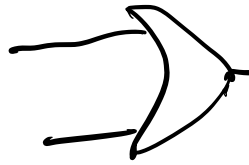

OR GATE

- output is 1 when at least one input is 1.


You can build a circuit for any boolean formula with NOT, AND, and OR gates.

Other commonly used gates:



NAND

(NOT AND)

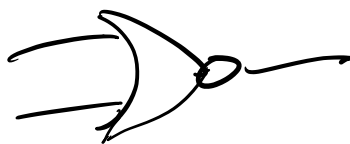

NOR

(NOT OR)

Building circuits for boolean formulas

" + " : OR

" • " : and


" \overline{A} " : not A

} notation w/in
boolean formulas

XOR :

$$A \text{ XOR } B = (A + B) \cdot \overline{(A \cdot B)}$$

Circuit:

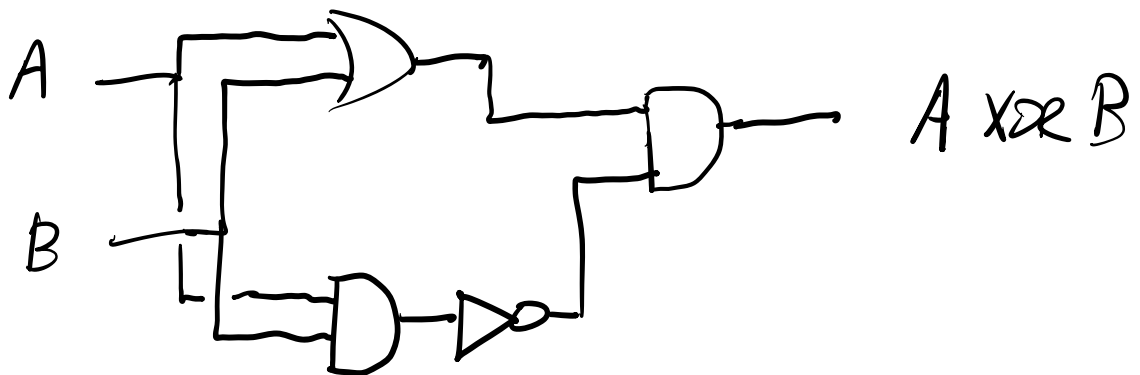

Another way to represent boolean functions is through truth tables

XOR

Write the inputs in increasing order in binary

A	B	Out
0	0	0
0	1	1
1	0	1
1	1	0

Multi-output truth tables


A	B	C	O1	O2
0	0	0	1	0
0	0	1	0	0
0	1	0	1	1
0	1	1	1	0
1	0	0	0	0
1	0	1	0	1
1	1	0	0	0
1	1	1	1	0

Algorithm for converting
a truth table to a circuit

- Repeat for each output:

- for each row in which
the output is 1, send
all inputs to an AND
gate, but negate those
inputs that are 0 first.

(e.g. first row above:

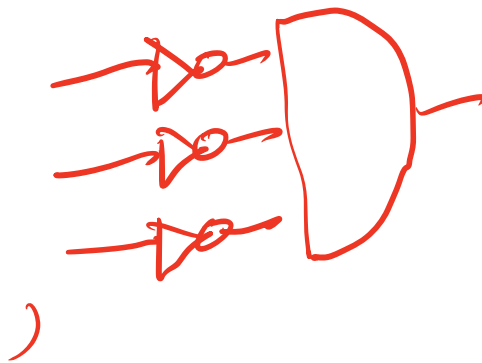


- take the outputs of the above AND gates for all the rows where the output is 1 and send them to an OR gate.
- the output of the OR gate is the desired output.

Two things to note:

- you can use a circle to represent negation of an input or output of a gate.




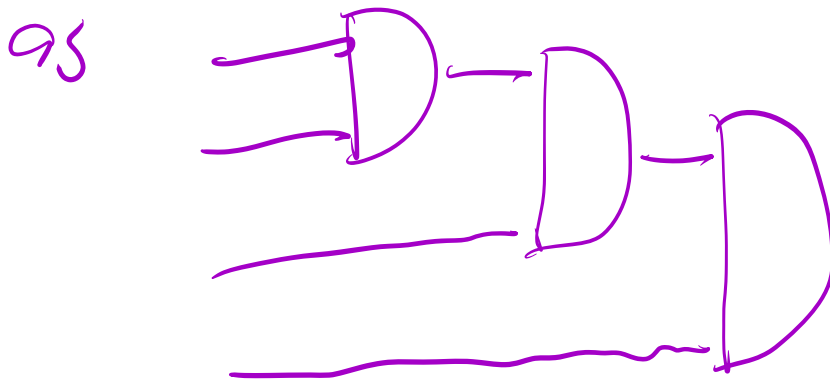- A multi-input
AND or OR gate
is built from a
sequence of AND
or OR gates:



Implementing the circuit for $O1$
(Output 1) in the above truth
table.

first row where $O1 = 1$

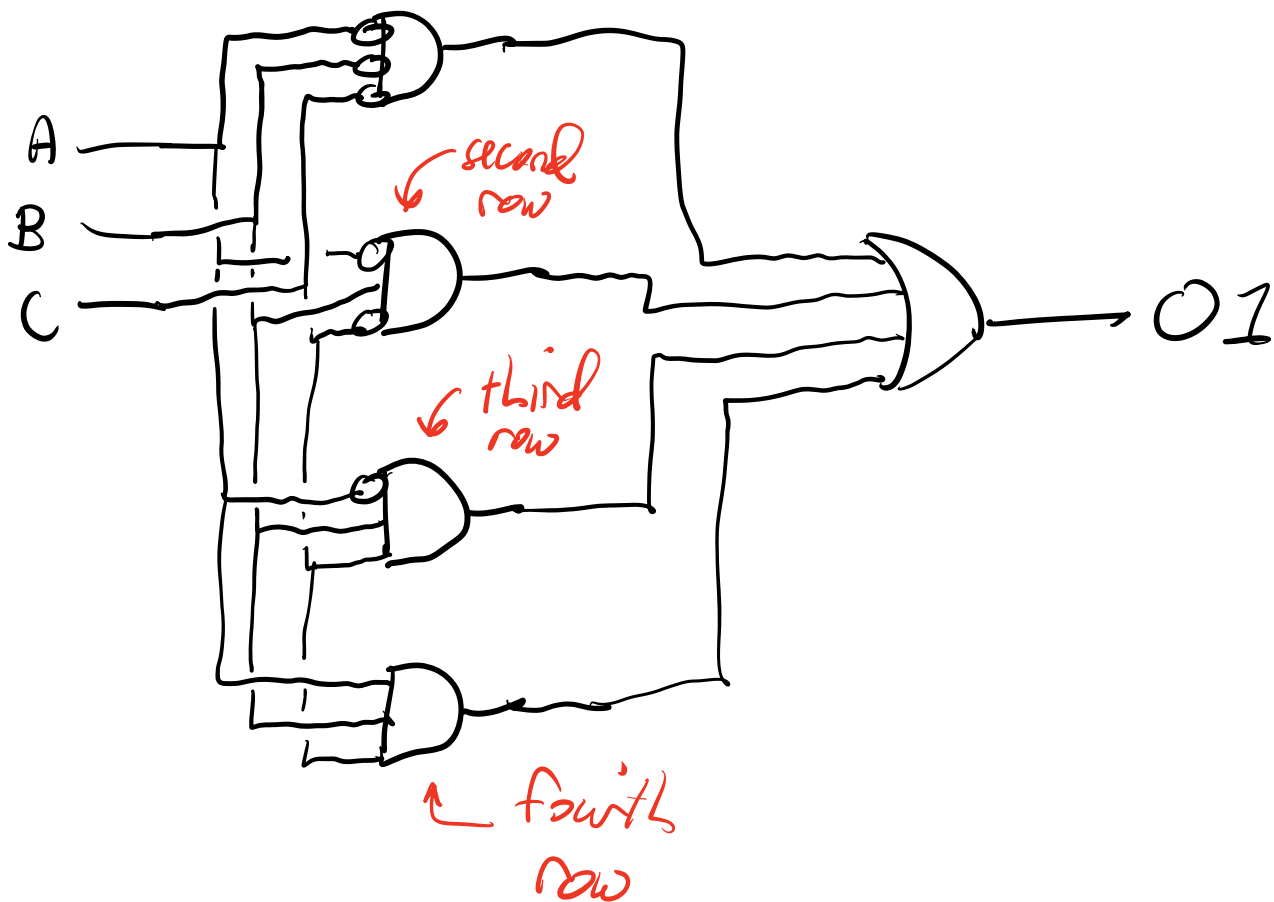

Combinational Circuit

- the output is determined by the current values of the inputs

Sequential Circuit

- outputs may depend on the values of the inputs at some previous time.


- retains state

- needed for storing data

(registers, memory, cache)

Useful combinational building blocks:

"Decoder"

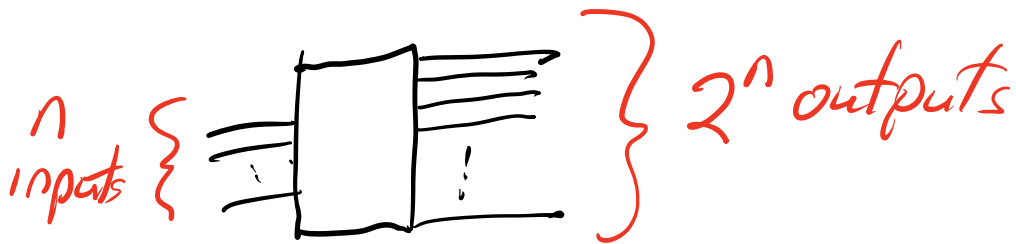

If the n inputs, when treated as an n -input binary, carries the value i , then the i^{th} output will be asserted (set to 1) and all other outputs will be 0.

1-bit decoder (1 input, 2 outputs)

