 


Where we left off: unclocked latch




$$S=1, R=0 \Rightarrow Q=1, \bar{Q}=0$$

$$S=0, R=1 \Rightarrow Q=0, \bar{Q}=1$$

$$S=0, R=0 \Rightarrow Q \text{ and } \bar{Q} \text{ hold their value.}$$

Adding a timing element: using the clock.


Clocked latch ("D-latch")

 

When clock = 0,
Q and \bar{Q} hold
their value.

When clock = 1,
Q gets the value
of D and \bar{Q}
gets the value of
 \bar{D} .


Draw as:

 

ignore \bar{Q}

"Flip Flop" - with falling edge trigger

- uses two D-latches:

 

↑ When clock=1, D flows into the left latch and the left latch's Q changes. However, at that point the C input to the right latch is ϕ , so the Q output of the right latch doesn't change.

- When clock falls to ϕ , no change occurs on the Q of the left latch.


However, the C input to the right latch becomes 1, so the Q output of the left latch flows into the D input of the right latch and is output on the right latch's Q.

The flip flop is the building block of registers & caches.


- "SRAM" (static mem)
- fast
- expensive (lots of transistors)

Now we'll use  to represent flip flop

 A 32-bit register consists of 32 flip flops:



Draw a register as:

 

"Register File"

- a collection of identical registers.

- e.g. `%rax`, `%rbx`, ...

- typically allows two reads and one write to registers at a time.


`addq %rax, %rsi`

just a number
↓
in machine code

- reading from `%rax` and `%rsi`, performs addition, writes result to `%rsi`.

Building a register file.

- assume 16 registers

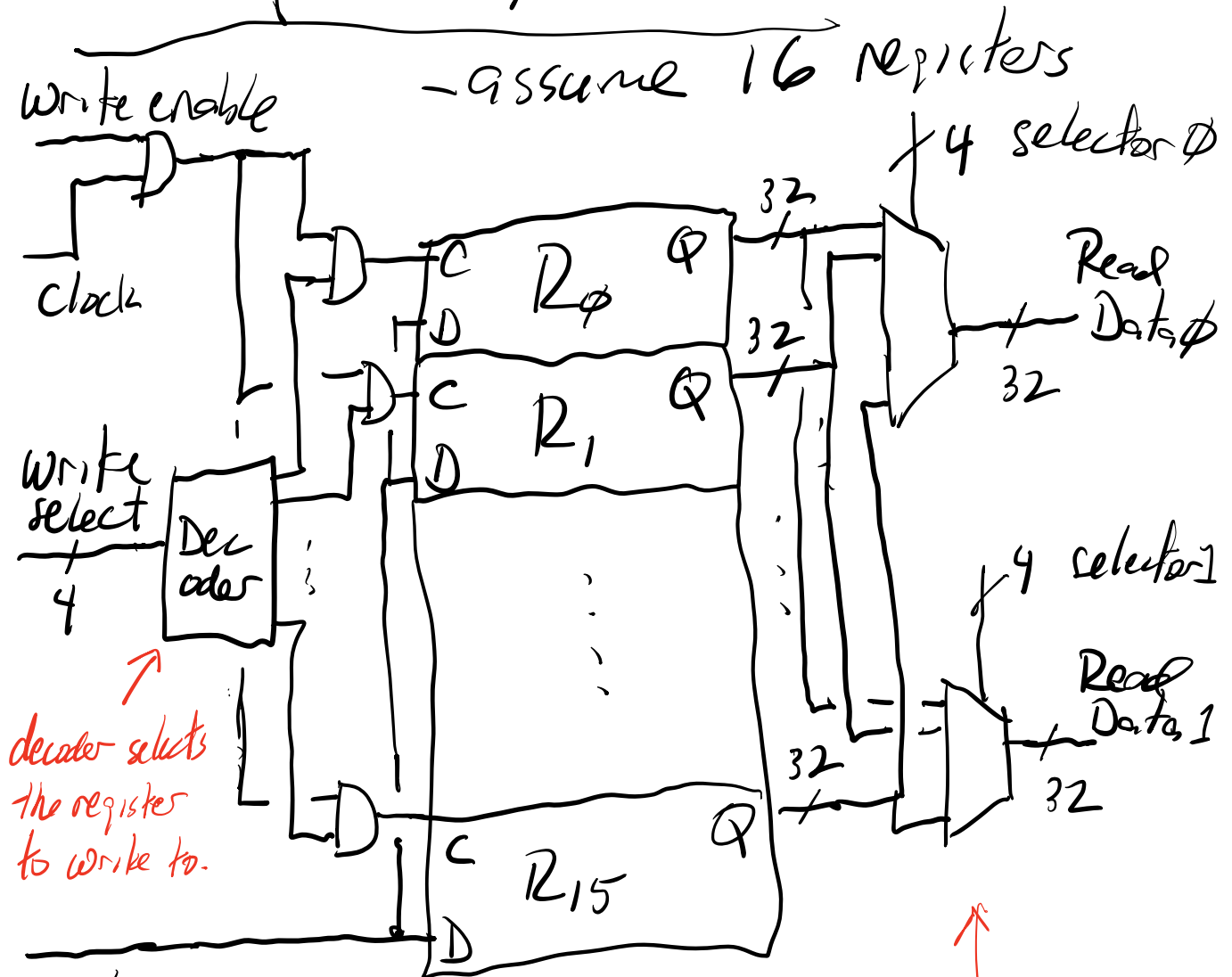

↑
decoder selects
the registers
to write to.

Write
data

↑ gets sent to the D input of every register.

↑
multiplexers select
the registers to
read from.

- A register can only change when:
 - the clock falls
 - write-enable = 1
 - write-select selects that register.
 - through the use of the decoder.
-

Main Memory is not made from Flip Flops.


- too expensive, not dense enough

Main memory uses "DRAM"

- dynamic RAM
- uses one transistor and one "capacitor" per bit.

↑
stores voltage
(tiny battery)

One DRAM cell (one bit)

 

When word line = 1, current will flow between the bit line and the capacitor.

When the capacitor holds a charge (high voltage), that represents a 1.

When the capacitor is discharged (low voltage), that represents a 0.

Setting word line = 1, bit line = 1, will cause current to flow from the bit to the capacitor, charging the capacitor - writing a 1.

Setting word line = 1, bit line = 0,
will cause current to flow from
the capacitor to the bit, discharging
from the capacitor.

- writing a 0.

To read, set word line = 1 and set
bit line to an intermediate voltage level.

If the voltage on bit line goes up, that
means the capacitor had held high
voltage and the current flowed from the
capacitor to the bit line.

- so, the value read is 1.

If the voltage on bit line goes down,
that means the capacitor held low voltage.

- the value read is 0.